 


Decoders

- Now, we'll look at some commonly used circuits: decoders and multiplexers.
 - These serve as examples of the circuit analysis and design techniques from last lecture.
 - They can be used to implement arbitrary functions.
 - We are introduced to abstraction and modularity as hardware design principles.
- Throughout the semester, we'll often use decoders and multiplexers as building blocks in designing more complex hardware.



What is a decoder

- In older days, the (good) printers used be like typewriters:
 - To print "A", a wheel turned, brought the "A" key up, which then was struck on the paper.
- Letters are encoded as 8 bit codes inside the computer.
 - When the particular combination of bits that encodes "A" is detected, we want to activate the output line corresponding to A
 - (Not actually how the wheels worked)
- How to do this "detection" : **decoder**
- General idea: given a k bit input,
 - Detect which of the 2^k combinations is represented
 - Produce 2^k outputs, only one of which is "1".

What a decoder does

- A **n-to- 2^n decoder** takes an n-bit input and produces 2^n outputs. The n inputs represent a binary number that determines which of the 2^n outputs is **uniquely** true.
- A 2-to-4 decoder operates according to the following truth table.
 - The 2-bit input is called S1S0, and the four outputs are Q0-Q3.
 - If the input is the binary number i, then output Qi is uniquely true.

| S1 | S0 | Q0 | Q1 | Q2 | Q3 |
|----|----|----|----|----|----|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |

- For instance, if the input S1 S0 = 10 (decimal 2), then output Q2 is true, and Q0, Q1, Q3 are all false.
- This circuit “decodes” a binary number into a “one-of-four” code.

How can you build a 2-to-4 decoder?

- Follow the design procedures from last time! We have a truth table, so we can write equations for each of the four outputs (Q0-Q3), based on the two inputs (S0-S1).

| S1 | S0 | Q0 | Q1 | Q2 | Q3 |
|----|----|----|----|----|----|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |

- In this case there's not much to be simplified. Here are the equations:

$$Q0 = S1' S0'$$


$$Q1 = S1' S0$$

$$Q2 = S1 S0'$$

$$Q3 = S1 S0$$

A picture of a 2-to-4 decoder

| S1 | S0 | Q0 | Q1 | Q2 | Q3 |
|----|----|----|----|----|----|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |

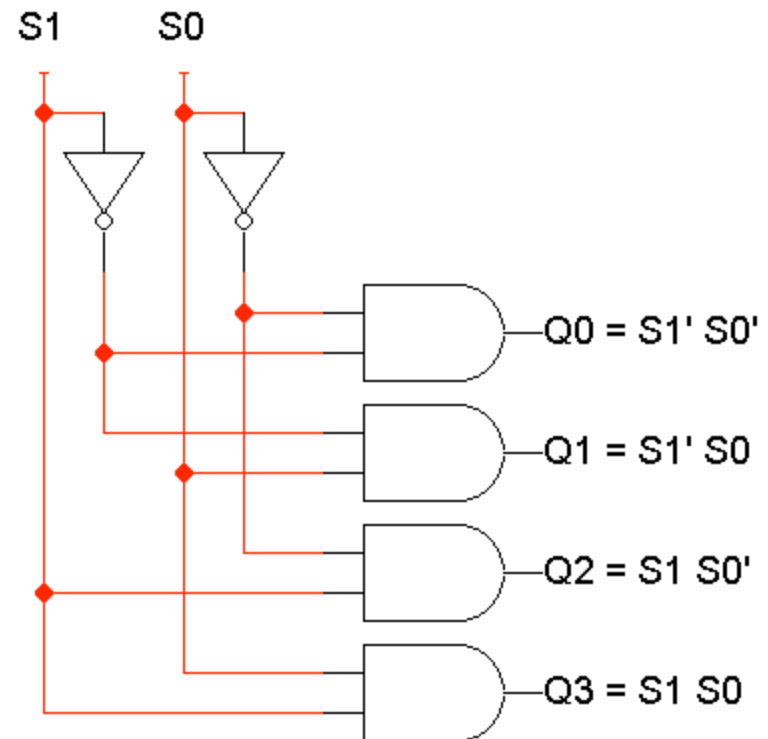

Enable inputs

- Many devices have an additional **enable input**, which is used to “activate” or “deactivate” the device.
- For a decoder,
 - EN=1 activates the decoder, so it behaves as specified earlier. Exactly one of the outputs will be 1.
 - EN=0 “deactivates” the decoder. By convention, that means **all** of the decoder’s outputs are 0.
- We can include this additional input in the decoder’s truth table:

| EN | S1 | S0 | Q0 | Q1 | Q2 | Q3 |
|----|----|----|----|----|----|----|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

An aside: abbreviated truth tables

- In this table, note that whenever $EN=0$, the outputs are always 0, **regardless** of inputs $S1$ and $S0$.



| EN | S1 | S0 | Q0 | Q1 | Q2 | Q3 |
|----|----|----|----|----|----|----|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

- We can abbreviate the table by writing x's in the input columns for $S1$ and $S0$.

| EN | S1 | S0 | Q0 | Q1 | Q2 | Q3 |
|----|----|----|----|----|----|----|
| 0 | x | x | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

Blocks and abstraction

  - Decoders are common enough that we want to encapsulate them and treat them as an individual entity.
- Block diagrams** for 2-to-4 decoders are shown here. The **names** of the inputs and outputs, not their order, is what matters.




$$\begin{aligned} Q0 &= S1' S0' \\ Q1 &= S1' S0 \\ Q2 &= S1 S0' \\ Q3 &= S1 S0 \end{aligned}$$

- A decoder block provides **abstraction**:
 - You can use the decoder as long as you know its truth table or equations, without knowing exactly what's inside.
 - It makes diagrams simpler by hiding the internal circuitry.
 - It simplifies hardware reuse. You don't have to keep rebuilding the decoder from scratch every time you need it.
- These blocks are like functions in programming!

A 3-to-8 decoder

 - Larger decoders are similar. Here is a 3-to-8 decoder.
 - The block symbol is on the right.
 - A truth table (without EN) is below.
 - Output equations are at the bottom right.
- Again, only one output is true for any input combination.



| S2 | S1 | S0 | Q0 | Q1 | Q2 | Q3 | Q4 | Q5 | Q6 | Q7 |
|----|----|----|----|----|----|----|----|----|----|----|
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |

$$Q0 = S2' S1' S0'$$

$$Q1 = S2' S1' S0$$

$$Q2 = S2' S1 S0'$$

$$Q3 = S2' S1 S0$$

$$Q4 = S2 S1' S0'$$

$$Q5 = S2 S1' S0$$

$$Q6 = S2 S1 S0'$$

$$Q7 = S2 S1 S0$$

So what good is a decoder?

- Do the truth table and equations look familiar?

| S1 | S0 | Q0 | Q1 | Q2 | Q3 |
|----|----|----|----|----|----|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |

$$Q0 = S1' S0'$$

$$Q1 = S1' S0$$

$$Q2 = S1 S0'$$

$$Q3 = S1 S0$$

- Decoders are sometimes called **minterm generators**.
 - For each of the input combinations, exactly one output is true.
 - Each output equation contains all of the input variables.
 - These properties hold for all sizes of decoders.
- This means that you can implement arbitrary functions with decoders. If you have a sum of minterms equation for a function, you can easily use a decoder (a minterm generator) to implement that function.

Design example: addition

- Let's make a circuit that adds three 1-bit inputs X , Y and Z .
- We will need two bits to represent the total; let's call them C and S , for "carry" and "sum." Note that C and S are two separate functions of the same inputs X , Y and Z .
- Here are a truth table and sum-of-minterms equations for C and S .

$0 + 1 + 1 = 10$ →


| X | Y | Z | C | S |
|-----|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

← $1 + 1 + 1 = 11$

$C(X,Y,Z) = \sum m(3,5,6,7)$
 $S(X,Y,Z) = \sum m(1,2,4,7)$

Decoder-based adder

 
- Here, two 3-to-8 decoders implement C and S as sums of minterms.



- The "+5V" symbol ("5 volts") is how you represent a constant 1 or true in LogicWorks. We use it here so the decoders are always active.

Using just one decoder

 - Since the two functions C and S both have the same inputs, we could use just one decoder instead of two.



$$C(X,Y,Z) = \sum m(3,5,6,7)$$

$$S(X,Y,Z) = \sum m(1,2,4,7)$$

Building a 3-to-8 decoder

- You could build a 3-to-8 decoder directly from the truth table and equations below, just like how we built the 2-to-4 decoder.
- Another way to design a decoder is to break it into smaller pieces.
- Notice some patterns in the table below:
 - When $S_2 = 0$, outputs Q_0 - Q_3 are generated as in a 2-to-4 decoder.
 - When $S_2 = 1$, outputs Q_4 - Q_7 are generated as in a 2-to-4 decoder.

| S2 | S1 | S0 | Q0 | Q1 | Q2 | Q3 | Q4 | Q5 | Q6 | Q7 |
|----|----|----|----|----|----|----|----|----|----|----|
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |

$$Q_0 = S_2' S_1' S_0' = m_0$$

$$Q_1 = S_2' S_1' S_0 = m_1$$

$$Q_2 = S_2' S_1 S_0' = m_2$$

$$Q_3 = S_2' S_1 S_0 = m_3$$

$$Q_4 = S_2 S_1' S_0' = m_4$$


$$Q_5 = S_2 S_1' S_0 = m_5$$

$$Q_6 = S_2 S_1 S_0' = m_6$$

$$Q_7 = S_2 S_1 S_0 = m_7$$

Decoder expansion

 
- You can use enable inputs to string decoders together. Here's a 3-to-8 decoder constructed from two 2-to-4 decoders:



| S2 | S1 | S0 | Q0 | Q1 | Q2 | Q3 | Q4 | Q5 | Q6 | Q7 |
|----|----|----|----|----|----|----|----|----|----|----|
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |

Modularity

 
- Be careful not to confuse the "inner" inputs and outputs of the 2-to-4 decoders with the "outer" inputs and outputs of the 3-to-8 decoder (which are in boldface).
- This is similar to having several functions in a program which all use a formal parameter "x".



- You could verify that this circuit is a 3-to-8 decoder, by using equations for the 2-to-4 decoders to derive equations for the 3-to-8.


A variation of the standard decoder

 - The decoders we've seen so far are **active-high** decoders.



| EN | S1 | S0 | Q0 | Q1 | Q2 | Q3 |
|----|----|----|----|----|----|----|
| 0 | x | x | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 |

 
- An **active-low decoder** is the same thing, but with an inverted EN input and inverted outputs.




| EN | S1 | S0 | Q0 | Q1 | Q2 | Q3 |
|----|----|----|----|----|----|----|
| 0 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | x | x | 1 | 1 | 1 | 1 |

Separated at birth?

 - Active-high decoders generate **minterms**, as we've already seen.



 
- The output equations for an active-low decoder are mysteriously similar, yet somehow different.



- It turns out that active-low decoders generate **maxterms**.

Active-low decoder example

 - So we can use active-low decoders to implement arbitrary functions too, but as a product of maxterms.
- For example, here is an implementation of the function from the previous page, $f(x,y,z) = \prod M(4,5,7)$, using an active-low decoder.



- The "ground" symbol connected to EN represents logical 0, so this decoder is always enabled.
- Remember that you need an AND gate for a product of sums.

Summary

- A n -to- 2^n decoder generates the minterms of an n -variable function.
 - As such, decoders can be used to implement arbitrary functions.
 - Later on we'll see other uses for decoders too.
- Some variations of the basic decoder include:
 - Adding an enable input.
 - Using active-low inputs and outputs to generate maxterms.
- We also talked about:
 - Applying our circuit analysis and design techniques to understand and work with decoders.
 - Using block symbols to encapsulate common circuits like decoders.
 - Building larger decoders from smaller ones.

How would you implement the function $f(x,y,z) = XZ'$ using a 3 to 8 decoder and a 2-input OR gate

- a) Outputs Q4 and Q6 of the decoder are connected to the OR gate
- b) Outputs Q2 and Q6 of the decoder are connected to the OR gate
- c) Outputs Q7 and Q6 of the decoder are connected to the OR gate
- d) Outputs Q4 and Q5 of the decoder are connected to the OR gate